

DEPARTMENT OF COMPUTER ENGINEERING,  
UNIVERSITY OF BENIN, BENIN CITY  
2016/2017 SESSION 2<sup>ND</sup> SEMESTER EXAMINATION

28/07/2017

CPE522: SYSTEM PROGRAMMING

Time: 3hours

ATTEMPT FIVE (5) QUESTIONS ONLY

1a architecture Behavioural of JK\_Flipflop is

--signal declaration.

signal qtemp, qbartemp : std\_logic := '0';

begin

Q <= qtemp

Qbar <= qbartemp

process(clk,reset)

begin

if(reset = '1') then

qtemp <= '0';

qbartemp <= '1';

elseif(rising\_edge(clk)) then

if(j = '0' and K = '0') then

NULL;

else(J = '0' and k = '1') then

qtemp <= '0';

qbartemp <= '1';

elseif(J = '1' and k = '0') then

qtemp <= '1';

qbartemp <= '0';

else

qtemp <= not temp;

qbartemp <= not qbartemp;

end if;

end if;

end process;

end Behavioral;

- i. Write the form of the process statement used in the behavioural description
- ii. Rewrite the description using the wait statement
- iii. Write and explain the form of the wait statement used
- iv. Rewrite the general form of the process statement for your answer to Qn1a ii
- v. What does the NULL statement, as used in the process statement, do?
- vi. Write the general form of the conditional control used in the process statement

(16marks)

- b. function and procedure are classified as subprograms in VHDL. Explain features that differentiate them

(4marks)

- 2a. Discuss the special characteristics of VHDL data pathways.  
 b. Consider the process statement of Qn2b

P1: Process

Variable B: integer := 1;

Begin

Loop1:

For A in 1 to 12 loop

B:= 400;

Loop2: loop

If B< (A\*\*2)

Exit loop2;

End if;

B:=B/A;

End loop loop2;

End loop loop1;

Wait;

End process

- i. Rewrite the process statement using the next statement.  
 ii. Write the syntax for the next statement. (15 marks)  
 c. Briefly discuss the 'wait' statement as used in VHDL. (5 marks)

- 3a. Write and explain the general syntax for a variable assignment (2 marks)  
 ai. List and define the basic concepts of hardware structure (3 marks)  
 b. Consider the device fig. Qn3b

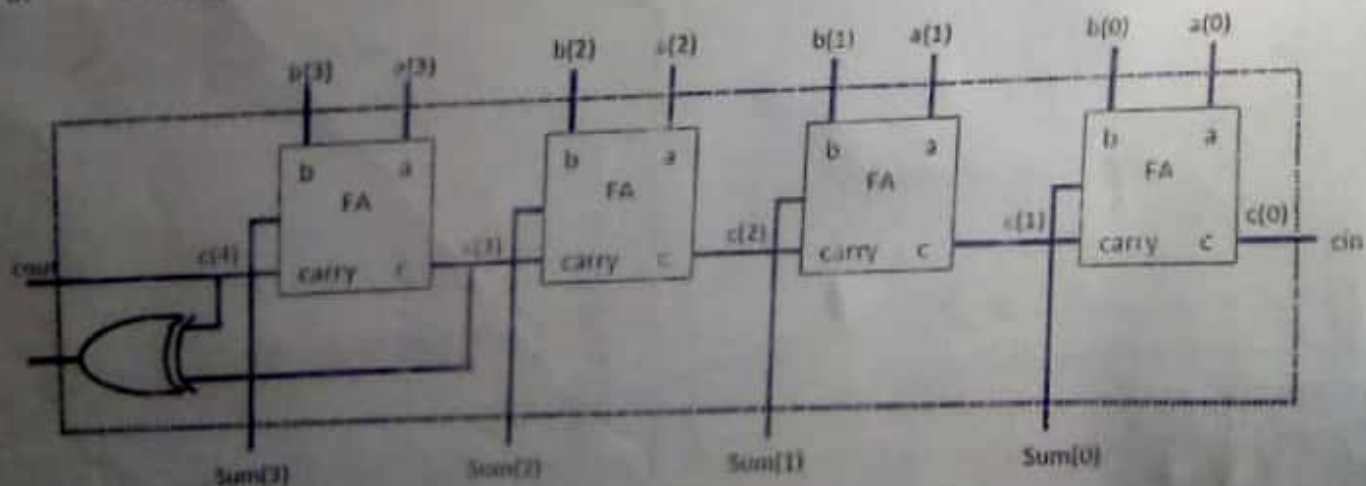


Fig. Qn3b

- i. Write a VHDL description for the components used as (a) building block(s) for the digital device of fig. Qn3b using behavioural description for architecture body.  
 ii. Write a structural description for fig. Qn3b using positional association for the component instantiation statement  
 (15 marks)

- 4a. Given the function  $f(X, Y, Z) = X\bar{Y}Z + \bar{X}Y\bar{Z} + \bar{X}YZ + XY\bar{Z}$   
 i. Sketch the logic circuit represented by the logic function.

architectural behaviour of 4-bit 1's  
 begin  
 process

Entity declaration

Entity Fig. Qn3b is

Port (Ain, bkin : in std\_logic;  
 Sumout, Cout : out std\_logic);

End entity;

architectural

variable - name := expression

Low cost approach  
 Programmability  
 Reconfigurability

- Write the entity declaration of the logic device assignment. (14 Marks)
- Sketch and define the components of a finite state machine. (6 marks)
- Design, using ROM, a square look up table for  $F(x) = \begin{cases} x^3, & \text{for } 0 \leq x \leq 1 \\ 0, & \text{Otherwise} \end{cases}$  (12 Marks)
- What is a look up table?
- What is a programmable logic device? (8 Marks)
- Distinguish between a PAL, ROM and PLA.
- Table Qn.6a below is the truth table of a code converter. Design a PAL logic implementation of the table. (14 Marks)
- Outline the advantages of PLDs. (6 Marks)
- The state diagram of a service machine is as shown in Fig.Qn7a
- Generate a state table for the machine
- Design a FSM
- What does this machine do? (15 Marks)
- Outline the advantages and disadvantages of FSMs (5 Marks)

Table Qn.6a: Code converter truth table

A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0
0	1	0	0	0	1	1	0
0	1	0	1	1	1	1	0
0	1	1	0	1	0	1	0
0	1	1	1	1	0	1	1
1	0	0	0	1	0	0	0
1	0	0	1	1	0	0	0
1	0	1	0	X	X	X	X
1	0	1	1	X	X	X	X
1	1	0	0	X	X	X	X
1	1	0	1	X	X	X	X
1	1	1	0	X	X	X	X
1	1	1	1	X	X	X	X


 


Fig.Qn.7a

N= Nickel = 5 Cents  
D = Dime = 10 Cents

 Each data path has a type associated with it, the type defines a range of values which may be passed over the pathway




DEPARTMENT OF COMPUTER ENGINEERING  
FACULTY OF ENGINEERING  
UNIVERSITY OF BENIN

SECOND SEMESTER EXAMINATION (2018/2019)

CPE522: DIGITAL SYSTEM DESIGN WITH VHDL 3HOURS


INSTRUCTIONS: ANSWER FIVE QUESTIONS IN ALL AND ATLEAST ONE FROM EACH SECTION

Q1. a) Consider the gate diagram below:

 

- i) Write a HDL program for the above device.
- ii) The output obtained from (i) above, should be convence to five different locations.
- b) If given constants "true" and "false" which can be used as fixed buses for 1's or 0's.
- i) Implement the HDL stub file for the constants in (b). Suppose we named the gate "WALLOP"
- ii) Draw the gate-diagram.
- (c) If a chip gate named "WIDGET" has a multiple outputs. Write an HDL stub file for defining the chip. (14marks)

 Q2. Consider the logic circuit of fig Qn 2(a) below:



- (i) Generate the truth table for the logic device
  - (ii) From the truth table, generate the logic function for the logic device
  - (iii) Write a HDL stub file for the device
- (14marks)

Q3. Explain briefly the following terms in relations to the structured design:

- i) Schematic circuit capture
- ii) Design process (simulation, synthesis)
- iii) Structural design decomposition
- iv) Design level


(14marks)

## SECTION B

- a) Lists four VHDL capabilities that you know (2marks)
- b) Write and explain the general syntax of the architecture body (4marks)
- c) Write a VHDL description for a 4:1 multiplexer using structural modelling (5marks)
- d) Write a VHDL program for an exclusive NOR gate using with-select statement (3marks)
- 
- a) Write a VHDL description for a full subtractor. Develop the sum of products of the Boolean equation (8marks)
- b) Write a VHDL description for an XOR gate using when-else statement (3marks)
- c) Write a VHDL program for RS flip-flop using behavioural modelling (3marks)

## SECTION C

 - a) With a suitable diagram describe the Mealy and Moore models of Finite State Machines (5marks)
- b) Use the classical design method to design a 0-to-7 counter (Tip clearly show the state diagram, transition table etc) (7marks)
- c) Use VHDL to redesign design the 0-to-7 counter in (b) and highlight the differences in the two design approaches (8marks)



- Q7. a) An alternative to state diagram representation for FSMs is the algorithm state machine. Discuss (5marks)
- b) Consider the VHDL code below. Manually synthesize the digital system (7marks)

```

ARCHITECTURE a3 OF mux2_1 IS
BEGIN
    OUT <= ((B AND NOT (SEL)) OR (A AND SEL));
END a3;
    
```

- c) Consider the VHDL code below
- Sketch the state diagram
  - Briefly describe the digital system

ARCHITECTURE a1 OF mux2\_1 IS

P1: PROCESS (sel, in0, in1)

BEGIN

IF (sel = '0') THEN

yout <= in0;

ELSE

yout <= in1;

END IF;

END P1;

END a1;

GOODLUCK

CPE522: SYSTEM PROGRAMMING

Time: 3 hours

28/10/2018

ATTEMPT FIVE (5) QUESTIONS ONLY

- 1a. A full sub-tractor implements the arithmetic equation  
 $D_i B_{out} = A - B - B_{in}$

Where  $D_i$  and  $B_{out}$  denote the difference and borrow functions respectively. Derive a canonical sum-of-products Boolean equation for each output.


- Draw the logic circuit.
- Write the entity declaration of the logic device.
- Write the architecture behavioural description for the device.
- Write the structural description for the device.

A	B	$B_{in}$	$D_i$	$B_{out}$
0	0	0	0	0
0	0	1	0	1
0	1	0	1	0
0	1	1	1	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	0
1	1	1	0	1

(12 marks)

 - b. Write an entity declaration for a device with the following ports:

Port D is a 12-bit bus, input only  
Port OE and CLK are each input bits  
Port AD is a 12-bit, bi-directional bus  
Port A is a 12-bit bus, output only  
Port INT is a three-state output  
Port AS is an output only



(4 marks)

(4 marks)

(12 marks)

- c. State the general form of an object declaration and explain.

- 2a. List and explain the major constructs in VHDL

- b. A two-to-one multiplexer has three data inputs, a, b, and c and two select control input, X and Y. The multiplexer has a single output Z. If  $X = 1$ , Z is equal to a. If  $Y = 1$ , Z is equal to b otherwise Z is equal to c

- Write an entity declaration for the multiplexer named mux. Express the process statement for the multiplexer. (5 marks)

- State the purposes that procedures serve in VHDL. (3 marks)

- 3a. List the characteristics of a process statement (4 marks)

- b. Consider the process statement below

Signal S: Integer := 0;

P1: PROCESS

Begin

S <= transport 1 after 1ns;

S <= transport 1 after 1ns, 2 after 3ns, 4 after 4ns, 7 after 5ns;

S <= transport 2 after 2ns;

S <= transport 3 after 5ns, 4 after 4ns, 4 after 5ns, 6 after 10ns;

Wait

End Process;

- What does this process statement do?
- What is the effect of the process statement on S?



Process statement

If X = 1 then  
Z = a

else if Y = 1 then  
Z = b

else Z = c  
(6 marks)




- A vhdl program controls a LED using a switch. When the switch is toggle to one (1) the reading (use will turn on when toggle to zero the reading (switch) will turn off.
- Briefly explain the behavior of the device described
  - Sketch the device described
  - Write the architecture description of the device using concurrent signal assignment statement (10marks)

4a. Consider the process statement of Qn4a

```

 P1: Process
Variable B: Integer:= 1;
Begin
Loop1:
  For A in 1 to 12 loop
    B:= 400;
    Loop2: loop
      If B < (A ** 2)
        Exit loop2;
      End if;
      B = B/A;
    End loop loop2;
  End loop loop1;
Wait;
End process
  
```



i. Rewrite the process statement using the while statement.

ii. Write the syntax for the while statement.

iii. Write the general form of the process statement used

(10marks)

b. Function and procedure are classified as subprograms in VHDL. Explain the features that differentiate them (3marks)

c. Write the general form of a VHDL function (3marks)

i. Write a VHDL "function" description for a 3-input exclusive OR function (4marks)

5a. Design, using ROM, a square look up table for  $F(x) = \begin{cases} 2x^2, & \text{for } 0 \leq x \leq 5 \\ 0, & \text{Otherwise} \end{cases}$

(12marks)

ii. What is a look up table?

bi. Outline the advantages of PLDs.

(8marks)

ii. Distinguish between a PAL, ROM and PLA.

6a. The state diagram of a service machine is as shown in Fig. Qn7a

i. Generate a state table for the machine

ii. Design a FSM for the service machine

(15marks)

iii. What does this machine do?

(5marks)

b. Outline the advantages and disadvantages of FSMs.

7. Consider a door combination lock FSM in Fig. Q7 with the following specification:



- When a user punches in 3 values in sequence, the door should open; if there is an error the lock must be reset; once the door opens the lock must be reset
- Inputs consist of sequence of input values, reset
- Outputs consists of door open/close
- Memory of the system must remember combination or always have it available as an input

- (a) i. Identify the number of states 5  
 ii. Describe each of the states and the corresponding transitions  
 identify the input and output of the FSM

(5marks)

- (b) Explain how you can come up with an optimal encoding scheme for the states  
 (c) Develop a state transition table for the FSM

(5marks)

(10marks)

 


Fig. Q7

Handwritten notes:

- State 1: closed
- State 2: closed
- State 3: closed
- State 4: open
- State 5: closed
- Input: reset, C1=value & new, C2=value & new, C3=value & new, ERR, not new
- Output: open, closed
- Initial state: S1
- Final state: S5
- Transitions: S1 to S2 (C1=value & new), S2 to S3 (C2=value & new), S3 to S5 (C3=value & new), S1 to S4 (ERR), S2 to S4 (ERR), S3 to S4 (ERR), S4 to S4 (ERR), S5 to S1 (not new)